

## Chapter: Electricity

### Key Definitions

- **Electric Current (I)** : The flow of electric charge in a conductor. It is measured in Amperes (A).
- **Voltage (V)** : The electric potential difference between two points. It is measured in Volts (V).
- **Resistance (R)** : The opposition to the flow of electric current. It is measured in Ohms (Ohm).
- **Ohm's Law** : The relationship between voltage, current, and resistance in a circuit, given by the formula:  
\$\$  
V = I \times R  
\$\$
- **Power (P)** : The rate at which electrical energy is consumed or converted. It is measured in Watts (W) and can be calculated using:

$$P = V \times I$$

\$\$

### Important Formulas

#### 1. Ohm's Law :

$$V = I \times R$$

\$\$

#### 2. Power in terms of resistance :

$$P = I^2 \times R$$

\$\$

or

$$P = \frac{V^2}{R}$$

\$\$

#### 3. Total Resistance in Series :

$$R_{\text{total}} = R_1 + R_2 + R_3 + \dots$$

\$\$

#### 4. Total Resistance in Parallel :

\$\$

$$1/R_{\text{total}} = 1/R_1 + 1/R_2 + 1/R_3 + \dots$$

\$\$

Diagrams

1. **Series Circuit** :

- Components are connected end-to-end.
- Current is the same through all components.
- Voltage is divided among components.

2. **Parallel Circuit** :

- Components are connected across the same two points.
- Voltage is the same across all components.
- Current is divided among the branches.

Summary Table

Quantity	Symbol	Unit
Electric Current	I	Amperes (A)
Voltage	V	Volts (V)
Resistance	R	Ohms (Ohm)
Power	P	Watts (W)

Key Takeaways

- Electric current is the flow of charge, and it requires a potential difference (voltage) to flow.
- Resistance affects how much current will flow for a given voltage.
- Ohm's Law is fundamental for understanding the relationship between voltage, current, and resistance.
- Power can be calculated in multiple ways depending on the known quantities.
- Understanding series and parallel circuits is crucial for analyzing complex electrical systems.