

# Physics — Electricity

## Chapter: Electricity

### Key Definitions

- **Electric Current:** The flow of electric charge in a conductor. It is measured in amperes (A).
- **Voltage (Potential Difference):** The difference in electric potential between two points. It is measured in volts (V).
- **Resistance:** The opposition to the flow of electric current. It is measured in ohms ( $\Omega$ ).
- **Ohm's Law:** The relationship between voltage (V), current (I), and resistance (R) in a circuit, stated as:

$$V = I \times R$$

- **Circuit:** A closed loop through which electric current can flow.
- **Conductor:** A material that allows the flow of electric current (e.g., copper).
- **Insulator:** A material that does not allow the flow of electric current (e.g., rubber).

### Important Formulas

1. **Ohm's Law:**

$$V = I \times R$$

2. **Power in Electrical Circuits:**

$$P = V \times I$$

Where ( P ) is power in watts (W), ( V ) is voltage in volts (V), and ( I ) is current in amperes (A).

3. **Resistance in Series:**

$$R_{total} = R_1 + R_2 + R_3 + \dots + R_n$$

4. **Resistance in Parallel:**

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

### Diagrams

- **Series Circuit:** A circuit where components are connected end-to-end, so the current flows through each component in turn.
- **Parallel Circuit:** A circuit where components are connected across common points or junctions, providing multiple paths for the current.

### Summary Table

Quantity	Symbol	Unit
Current	I	Amperes (A)

Quantity	Symbol	Unit
Voltage	V	Volts (V)
Resistance R		Ohms ( $\Omega$ )
Power	P	Watts (W)

### Key Takeaways

- Electric current is the flow of charge, and it requires a closed circuit to flow.
- Voltage is the driving force that pushes the current through the circuit.
- Resistance opposes the flow of current, and it can be calculated using Ohm's Law.
- Components in a circuit can be arranged in series or parallel, affecting the total resistance and current flow.
- Understanding these concepts is crucial for analyzing and designing electrical circuits.